



Department of Technology

Coursework report

Coursework Title:	Second Mandatory Assignment--VHDL Programing (Autumn 2015)
Date of Submission:	No. 19. 2015
I hereby certify that the work described in this report is my own work.	

Submitted by

Name of the Student:	Qinghui Liu (Brian Liu)
Student Number:	888087
Email Address:	qinghui.liu@student.hbv.no
Date of Completion:	Nov. 17, 2015

ABSTRACT

This report is about the solutions on the secondary assignment – VHDL programming (autumn 2015), which mainly contains two parts: one is theoretical part, and another one is practical part.

Theoretical part is a problem that need to identify all errors contained in given VHDL code.

Practical part contains 6 VHDL programming tasks as below:

1. Implement an ALU capable of performing from 8 to 15 different operations.
2. Implement a 16 to 4 multiplexer that receives four vectors of four elements each and transmits one of those four-element vector at a time.
3. Implement a four digits common anode BCD to seven-segment display decoder.
4. Use 2 and 3 as components to implement the four-digit seven-segment display decoder.
5. Use a full-adder as component (implemented in one single file) to implement a four-bit ripple-carry adder.
6. Repeat 5, but implementing a four-bit ripple-carry adder/subtractor instead.

This report will give detail solutions to each question and task.

Table of Contents

Abstract	2
VHDL Introduction	5
VHDL Overview	5
ENTITY	5
ARCHITECTURE	5
Test Bench	5
1 Theoretical Part	6
List of errors:	6
Correct Code	6
2. Practical Part	7
1. ALU design	7
Overview	7
32-Bit ALU Block Diagram	7
Table of ALU Operations Sepcification	8
Entity of ALU	8
Architecture of ALU	9
Simulation	10
2. Multiplexer 16 to 4	11
Overview	11
VHDL Code	11
Simulation	12
3. BCD to 7-Segment Display	13
Overview	13
VHDL Code	14
Simulation	14
4. Four-Digit Seven-Segment Display Decoder	15
Overview	15
VHDL Code	16
Simulation	17

5. Four-Bit Ripple-Carry Adder	18
Overview	18
VHDL Code	18
Simulation	19
6. Four-Bit Ripple-Carry Adder/Subtractor	20
Overview	20
VHDL Code	20
Simulation	21
Conclusion	22
References	22
Appendices	22

VHDL OVERVIEW

VHDL consists of an entity which can contain other entities as components of the top-level entity. Each entity is modeled by an entity declaration and an architecture body, as Fig. 1.0.

 


Fig. 1.0 VHDL Model

ENTITY

An ENTITY represents a template for a hardware block. It describes just the outside view of a hardware module – namely its interface with other modules in terms of input and output signals.

The inner operation of the entity is described by an ARCHITECTURE associated with it.

ARCHITECTURE

An ARCHITECTURE describes how an ENTITY operates. It can describe an entity in a structural style, behavioural style or mixed style.

TEST BENCH

To simulate a design containing a core, create a test bench file. The test bench should instantiate the top level module and should contain stimuli to drive the input ports of the design.

1 THEORETICAL PART

LIST OF ERRORS:

- o Line 3: should remove comment, need use IEEE.numeric_std.ALL;
- o Line 5: missing 'is' at the end of line
- o Line 7: missing ';' at the end of line
- o Line 9: misplacing ';' before the last '}', and missing ';' at the end of line
- o Line 10: missing ';' at the end of line
- o Line 13: missing '>' before 'o'
- o Line 15: 'Q' is incompatible with 'tmp', the right statement should be "Q <= std_logic_vector(tmp);"
- o Line 16: process() missing sensitivity list, should be -- process (CLK, CLR)
- o Line 19: "CLR = 1" is wrong, should be "if(CLR = '1') and missing "then" at the end of line
- o Line 24: should use "else" instead of "elsif"
- o Line 28: should use "end process;"

CORRECT CODE

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.numeric_std.ALL;
4
5  entity counter_bin is
6      generic (N: integer := 4;
7              M : integer := 10);
8      port ( CLK, CLR : in STD_LOGIC;
9            Q : out STD_LOGIC_VECTOR (N-1 downto 0));
10 end counter_bin;
11
12 architecture Behavioral of counter_bin is
13     signal tmp : unsigned (N-1 downto 0) := (others => '0');
14 begin
15     Q <= std_logic_vector(tmp);
16     process (CLK, CLR)
17     begin
18         if (CLK'event and CLK = '1') then
19             if (CLR = '1') then
20                 tmp <= (others => '0');
21             elsif (tmp = (M-1)) then
22                 tmp <= (others => '0');
23             else
24                 tmp <= tmp +1;
25             end if;
26         end if;
27     end process;
28 end Behavioral;
29
```

2. PRACTICAL PART

1. ALU DESIGN

OVERVIEW

An Arithmetic/Logic Unit (ALU) is a multipurpose device capable of providing several different arithmetic and logic operations. The specific operation to be performed can be chosen by the mode select inputs.

ALU is a fundamental building block of many types of computing circuits, including the central processing unit (CPU) of computers, FPU, and graphics processing units (GPUs). A single CPU, FPU or GPU may contain multiple ALUs. (Wikipedia, n.d.)

32-BIT ALU BLOCK DIAGRAM

The ALU will be designed has 4 inputs: **clk**, **A(32)**, **B(32)**, **opco(4)**, and 2 outputs: **Y(32)** and **nzco(4)**. As Fig. 1.1.

The **clk** input is clock signal which rising edge can trigger operations. The ALU operation is specified by the **opco(4)** input. **A** and **B** input store the two operands for ALU.

The **Y(32)** output stores the operation result specified by **opco(4)** input. The **nzco(4)** output contains flag values:

- **nzco(3)**: "Negative" flag, which indicates the result of an arithmetic operation is negative.
- **nzco(2)**: "Zero" flag, which indicates all bits of the Y bus are logic zero.
- **nzco(1)**: "Carry" flag, which conveys the carry or borrow resulting from an addition/subtraction.
- **nzco(0)**: "Overflow" flag, which indicates the result has exceeded the range of the Y bus.

 


Fig. 1.1 ALU Diagram

TABLE OF ALU OPERATIONS SEPCIFICATION

NO.	Opcode	Function	Description
1	0000	Addition	$Y \leq A + B$
2	0001	Subtraction	$Y \leq A - B$
3	0010	Increment A	$Y \leq A + 1$
4	0011	Increment B	$Y \leq B + 1$
5	0100	Decrement A	$Y \leq A - 1$
6	0101	Decrement B	$Y \leq B - 1$
7	0110	Transfer A	$Y \leq A$
8	0111	Transfer B	$Y \leq B$
9	1000	AND	$Y \leq A \text{ and } B$
10	1001	OR	$Y \leq A \text{ or } B$
11	1010	NOT A	$Y \leq \text{not } A$
12	1011	NOT B	$Y \leq \text{not } B$
13	1100	A NAND B	$Y \leq A \text{ nand } B$
14	1101	A NOR B	$Y \leq A \text{ nor } B$
15	1110	A XOR B	$Y \leq A \text{ xor } B$
16	1111	A EX-NOR B	$Y \leq \text{not } (A \text{ xor } B)$

Fig. 1.2 ALU Operations Spec.

ENTITY OF ALU

```

20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 use IEEE.STD_LOGIC_unsigned.ALL;
23
24 entity ALU is
25     generic (TOTAL_BITS : natural := 32);
26     port (
27         clk      : in  std_logic;
28         opco     : in  std_logic_vector(3 downto 0);
29         A        : in  std_logic_vector(TOTAL_BITS - 1 downto 0);
30         B        : in  std_logic_vector(TOTAL_BITS - 1 downto 0);
31         Y        : out std_logic_vector(TOTAL_BITS - 1 downto 0);
32         nzco     : out std_logic_vector(3 downto 0)
33     );
34 end ALU;
```

 


Fig. 1.4 Entity of 32-bit ALU

ARCHITECTURE OF ALU

```

36 architecture alu_arc of ALU is
37 begin
38     process (clk,A,B,opco)
39         variable temp : std_logic_vector(TOTAL_BITS downto 0) := (others =>'0');
40         variable yv: std_logic_vector(TOTAL_BITS-1 downto 0);
41         variable cfv, zfv: std_logic;
42     begin
43         zfv := '0';
44         if rising_edge(clk) then
45             case opco is
46                 when "0000" => -- A+B
47                     temp := ('0' & A) + ('0' & B);
48                     yv := temp(TOTAL_BITS-1 downto 0);
49                     cfv:= temp(TOTAL_BITS);
50                     nzco(0) <= yv(TOTAL_BITS-1)
51                         xor cfv
52                         xor A(TOTAL_BITS -1)
53                         xor B(TOTAL_BITS -1);
54                     nzco(1) <= cfv;
55                 when "0001" => -- A-B
56                     temp := ('0' & A) - ('0' & B);
57                     yv := temp(TOTAL_BITS-1 downto 0);
58                     cfv:= temp(TOTAL_BITS);
59                     nzco(0) <= yv(TOTAL_BITS-1)
60                         xor cfv
61                         xor A(TOTAL_BITS -1)
62                         xor B(TOTAL_BITS -1);
63                     nzco(1) <= cfv;
64                 when "0010" => -- A+1
65                     temp := ('0' & A) + 1;
66                     yv := temp(TOTAL_BITS-1 downto 0);
67                     cfv:= temp(TOTAL_BITS);
68                     nzco(0) <= yv(TOTAL_BITS-1)
69                         xor cfv
70                         xor A(TOTAL_BITS -1);
71                     nzco(1) <= cfv;
72                 when "0011" => -- B+1
73                     temp := ('0' & B) + 1;
74                     yv := temp(TOTAL_BITS-1 downto 0);
75                     cfv:= temp(TOTAL_BITS);
76                     nzco(0) <= yv(TOTAL_BITS-1)
77                         xor cfv
78                         xor B(TOTAL_BITS -1);
79                     nzco(1) <= cfv;
80                 when "0100" => -- A-1
81                     temp := ('0' & A) - 1;
82                     yv := temp(TOTAL_BITS-1 downto 0);
83                     cfv:= temp(TOTAL_BITS);
84                     nzco(0) <= yv(TOTAL_BITS-1)
85                         xor cfv
86                         xor A(TOTAL_BITS -1);
87                     nzco(1) <= cfv;
88
114                 when "1111" => -- EX-NOR
115                     yv := not (A xor B);
116                 when others =>
117                     yv := A;
118             end case;
119
120             for i in 0 to TOTAL_BITS-1 loop
121                 zfv:= zfv or yv(i);
122             end loop;
123
124             y <= yv;
125             nzco(2) <= not zfv;
126             nzco(3) <= yv(TOTAL_BITS-1);
127         end if;
128     end process;
129 end alu_arc;

```

Fig. 1.5 Architecture of 32-bit ALU

SIMULATION

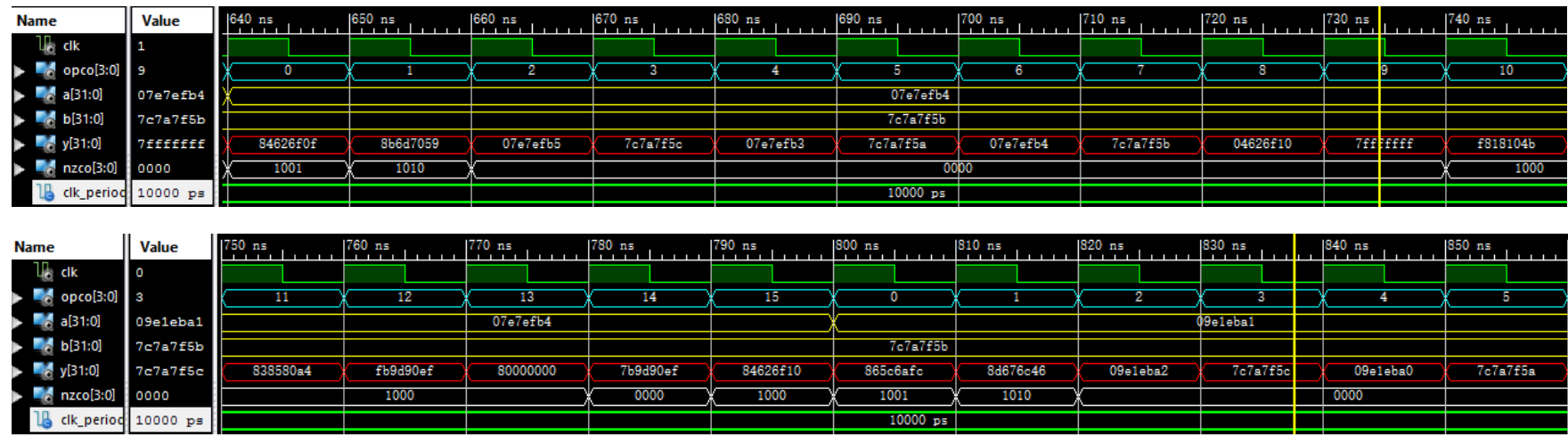


Fig. 1.6 ALU Simulation Results

```

64  -- Clock process definitions
65  clk_process :process
66  begin
67      wait for clk_period/2;
68      clk <= not clk;
69  end process clk_process;
70
71
72  -- Stimulus process
73  opco_proc: process
74  begin
75      wait for clk_period;
76      opco <= opco+1;
77  end process opco_proc;
78
79  ab_proc: process
80  begin
81      b <= X"7C7A7F5B";
82      wait for clk_period*16;
83      a <= a+X"01F9FBED";
84  end process ab_proc;

```

Fig. 1.7 ALU Test Bench Code

2. MULTIPLEXER 16 TO 4

OVERVIEW

A multiplexer (or mux) is a device that selects one of several analog or digital input signals and forwards the selected input into a single line.

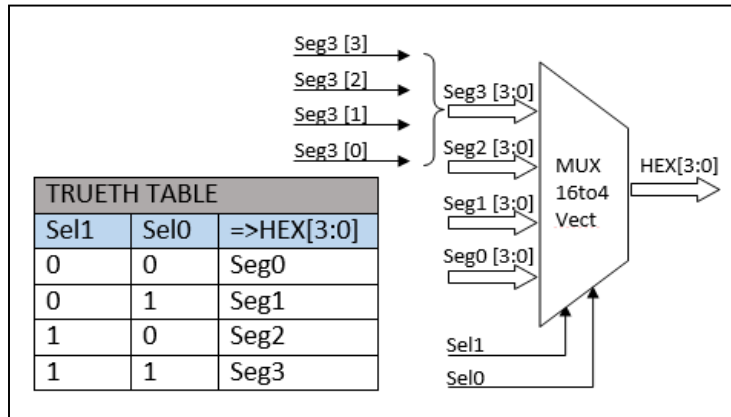


Fig. 2.1 True Table of Mux 16 to 4

VHDL CODE

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity Mux16to4v is
5     Port ( Seg0, Seg1, Seg2, Seg3 : in STD_LOGIC_VECTOR (3 downto 0);
6           Sel : in STD_LOGIC_VECTOR (1 downto 0);
7           HEX : out STD_LOGIC_VECTOR (3 downto 0));
8 end Mux16to4v;
9
10 architecture Behavioral of Mux16to4v is
11
12 begin
13     HEX <= Seg0 when Sel="00" else
14             Seg1 when Sel="01" else
15             Seg2 when Sel="10" else
16             Seg3 ;
17
18 end Behavioral;
```

 


Fig. 2.2 VHDL Code of Mux 16 to 4

SIMULATION

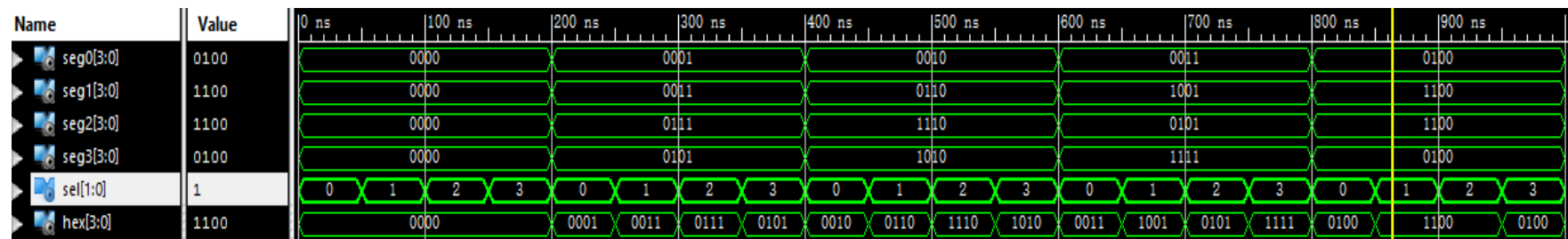


Fig. 2.3 Simulation Results of Mux16to4

```

54  -- Stimulus process
55  stim_proc_sel: process
56  begin
57      wait for 50 ns;
58      sel <= sel + 1;
59  end process;
60
61  stim_proc_seg: process
62  begin
63      wait for 200 ns;
64      seg0 <= seg0+1;
65      seg1 <= seg1+3;
66      seg2 <= seg2+7;
67      seg3 <= seg3+5;
68  end process;

```

Fig. 2.4 Mux16to4 Test Bench

3. BCD TO 7-SEGMENT DISPLAY

OVERVIEW

Binary Coded Decimal (BCD) to 7-Segment Display Decoder provides a very convenient way of displaying information or digital data with 7-segment LED (Light Emitting Diode), as Fig. 3.1

A standard 7-segment LED display generally has 8 input connections, one for each LED segment and one that acts as a common terminal or connection for all the internal display segments. Some single displays have also have an additional input pin to display a decimal point in their lower right or left hand corner.

There are two important types of 7-segment LED digital display.

- The Common Cathode Display (CCD)
- The Common Anode Display (CAD)

They can be made to display a variety of numbers or characters, as Fig. 3.2

 


Fig. 3.2 7-Segment Display Elements

A truth table can be giving the segments that need to be illuminated in order to produce the required character as shown below, as Fig 3.3

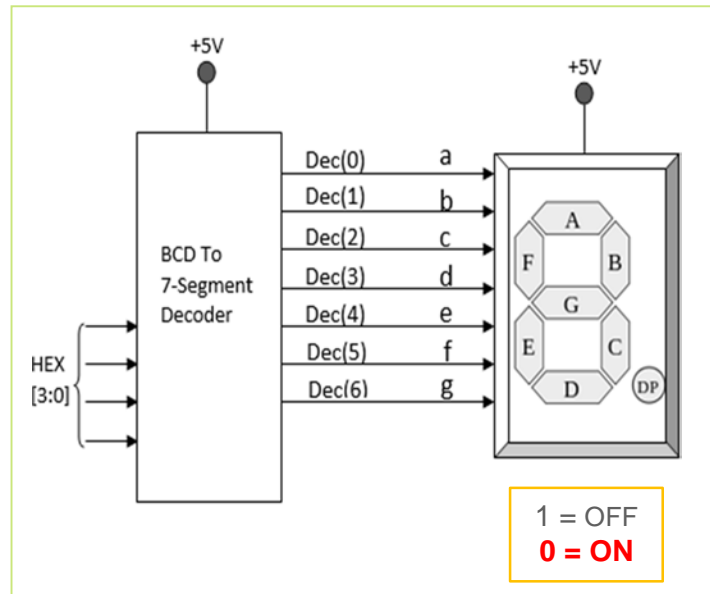


Fig. 3.1 BCD to 7-Segment Decoder

Character	a	b	c	d	e	f	g
0	0	0	0	0	0	0	1
1	1	0	0	1	1	1	1
2	0	0	1	0	0	1	0
3	0	0	0	0	1	1	0
4	1	0	0	1	1	0	0
5	0	1	0	0	1	0	0
6	0	1	0	0	0	0	0
7	0	0	0	1	1	1	1
8	0	0	0	0	0	0	0
9	0	0	0	0	1	0	0
A	0	0	0	1	0	0	0
b	1	1	0	0	0	0	0
C	0	1	1	0	0	0	1
d	1	0	0	0	0	1	0
E	0	1	1	0	0	0	0
F	0	1	1	1	0	0	0

Fig. 3.3 Truth Table for a 7-segment display

VHDL CODE

```

4  entity BCDto7seg is
5      Port ( HEX : in  STD_LOGIC_VECTOR(3 downto 0);
6            Dec : out STD_LOGIC_VECTOR(6 downto 0)
7            );
8  end BCDto7seg;

10 architecture BCD_arc of BCDto7seg is
11     signal digit : std_logic_vector(6 downto 0);
12 begin
13     process (HEX)
14         variable sel : std_logic_vector(3 downto 0);
15     begin
16         sel := HEX;
17         case sel is
18             when x"0" => digit <= "0000001";--display_0;
19             when x"1" => digit <= "1001111";--display_1;
20             when x"2" => digit <= "0010010";--display_2;
21             when x"3" => digit <= "0000110";--display_3;
22             when x"4" => digit <= "1001100";--display_4;
23             when x"5" => digit <= "0100100";--display_5;
24             when x"6" => digit <= "0100000";--display_6;
25             when x"7" => digit <= "0001111";--display_7;
26             when x"8" => digit <= "0000000";--display_8;
27             when x"9" => digit <= "0000100";--display_9;
28             when x"A" => digit <= "0001000";--display_A;
29             when x"B" => digit <= "1100000";--display_b;
30             when x"C" => digit <= "0110001";--display_C;
31             when x"D" => digit <= "1000010";--display_d;
32             when x"E" => digit <= "0110000";--display_E;
33             when others => digit <= "0111000";--display_F;
34         end case;
35     end process;
36     Dec<= digit;
37 end BCD_arc;

```

 


Fig. 3.4 BCDto7Seg Code

SIMULATION

 


Fig. 3.5 Simulation Results

```

41  -- Stimulus process
42  stim_proc: process
43  begin
44      wait for 50 ns;
45      HEX <= HEX + 1;
46  end process;

```

Fig. 3.6 BCDto7Seg Test Bench

4. FOUR-DIGIT SEVEN-SEGMENT DISPLAY DECODER

OVERVIEW

This decoder contains several different parts. A counter is provided to provide the timing for the anode select lines (AN₃-AN₀). The two bits of the counter are also used to select the digit (and digit point) that is driven on the display. Using the top-two bits of a binary counter ensures that each digit will be driven for the same amount of time, as Fig. 4.1

This decoder also contains two multiplexers. One multiplexer is used to select the appropriate 4-bit segment input to display. This is a 4-bit, 4 to 1 multiplexer. The second multiplexer is used to select the appropriate decimal point to display. The controller also contains two decoders: one decoder is used to decode the four-bit value into the seven segment signals and the second decoder is used to decode the two-bit anode_select signal and generate the four independent anode control signals.

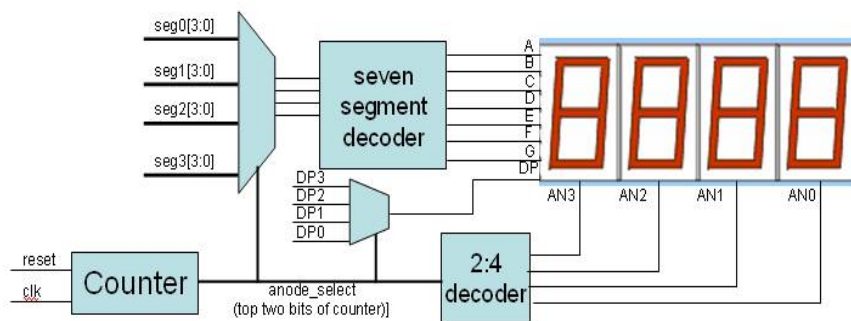


Fig. 4.1 Four_Bit-7Seg-Display Diagram

 


Fig. 4.2 Four_Bit-7Seg-Decoder

VHDL CODE


```

1  --- define component 2to4 decoder for anode_select
2  library IEEE;
3  use IEEE.STD_LOGIC_1164.ALL;
4
5  entity Decoder2to4 is
6  port(
7      A : in std_logic_vector(1 downto 0);
8      AN : out std_logic_vector(3 downto 0)
9  );
10 end Decoder2to4;
11
12 architecture dec_arc of Decoder2to4 is
13 begin
14     AN <= "1110" when A="00" else
15           "1101" when A="01" else
16           "1011" when A="10" else
17           "0111";
18 end dec_arc;
19
20 --- define component Mux4to1 for dp_select
21 library IEEE;
22 use IEEE.STD_LOGIC_1164.ALL;
23
24 entity Mux4to1 is
25 port(
26     inp : in std_logic_vector(3 downto 0);
27     sel : in std_logic_vector(1 downto 0);
28     oup : out std_logic
29 );
30 end Mux4to1;
31
32 architecture mux4_arc of Mux4to1 is
33 begin
34     with sel select
35         oup <= inp(3) when "00",
36                inp(2) when "01",
37                inp(1) when "10",
38                inp(0) when others;
39 end mux4_arc;
40
41 --- define component Mux16to4vector for digit_select
42 library IEEE;
43 use IEEE.STD_LOGIC_1164.ALL;
44
45 entity Mux16to4 is
46 port(
47     seg0, seg1, seg2, seg3 : in std_logic_vector(3 downto 0);
48     sel : in std_logic_vector(1 downto 0);
49     o_hex : out std_logic_vector(3 downto 0)
50 );
51 end Mux16to4;
52
53 architecture mux16_arc of Mux16to4 is
54 begin
55     with sel select
56         o_hex <= seg0 when "00",
57                seg1 when "01",
58                seg2 when "10",
59                seg3 when others;
60 end mux16_arc;
61
62
63
64
65
66
67
68
69
70
71
72
73
74
75
76
77
78
79
80
81
82
83
84
85
86
87
88
89
90
91
92
93
94
95
96
97
98
99
100
101
102
103
104
105
106
107 --- build 4 digit 7-segment display
108 library IEEE;
109 use IEEE.STD_LOGIC_1164.ALL;
110 use IEEE.STD_LOGIC_UNSIGNED.ALL;
111 use IEEE.numeric_std.ALL;
112
113 entity fd7d is
114 port (
115     clk: in std_logic;
116     seg0, seg1, seg2, seg3 : in std_logic_vector(3 downto 0);
117     DP : in std_logic_vector(3 downto 0);
118     segments : out std_logic_vector(6 downto 0);
119     dp_out : out std_logic;
120     an_out : out std_logic_vector(3 downto 0)
121 );
122
123 end fd7d;
124
125 architecture Behavioral of fd7d is
126     COMPONENT Mux4to1
127     PORT(
128         inp : IN std_logic_vector(3 downto 0);
129         sel : IN std_logic_vector(1 downto 0);
130         oup : OUT std_logic
131     );
132     END COMPONENT;
133     COMPONENT Mux16to4
134     PORT(
135         seg0 : IN std_logic_vector(3 downto 0);
136         seg1 : IN std_logic_vector(3 downto 0);
137         seg2 : IN std_logic_vector(3 downto 0);
138         seg3 : IN std_logic_vector(3 downto 0);
139         sel : IN std_logic_vector(1 downto 0);
140         o_hex : OUT std_logic_vector(3 downto 0)
141     );
142     END COMPONENT;
143     COMPONENT Decoder2to4
144     PORT(
145         A : IN std_logic_vector(1 downto 0);
146         AN : OUT std_logic_vector(3 downto 0)
147     );
148     END COMPONENT;
149     COMPONENT BCDto7seg
150     PORT(
151         HEX : IN std_logic_vector(3 downto 0);
152         Dec : OUT std_logic_vector(6 downto 0)
153     );
154     END COMPONENT;
155
156     signal hex_in : std_logic_vector(3 downto 0);
157
158 begin
159     sel_pro: process(clk)
160     begin
161         if ( clk'EVENT and clk = '1' ) then
162             sel <= sel + '1';
163         end if;
164     end process ;
165
166     comp0: Decoder2to4 port map(sel, an_out);
167     comp1: Mux16to4 port map(seg0, seg1, seg2, seg3,
168                             sel, hex_in);
169     comp2: BCDto7seg port map(hex_in, segments);
170     comp3: Mux4to1 port map(DP, sel, dp_out);
171
172 end Behavioral;
173

```

Fig. 4.3 Part of VHDL code for fd7d

SIMULATION

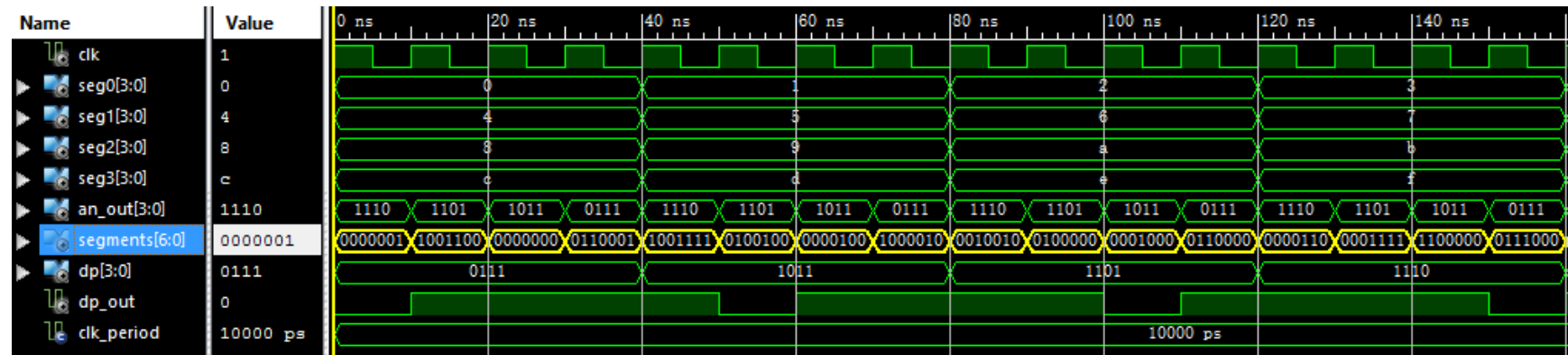

```

68  -- Clock process definitions
69  clk_process :process
70  begin
71      wait for clk_period/2;
72      clk <= not (clk);
73  end process clk_process;
74
75  -- segment process definitions
76  seg_proc: process
77  begin
78      wait for 4*clk_period;
79      seg0 <= seg0 + 1;
80      seg1 <= seg1 + 1;
81      seg2 <= seg2 + 1;
82      seg3 <= seg3 + 1;
83
84  end process seg_proc;

```

```

86  -- dp input process definitions
87  dp_proc: process (seg0, seg1, seg2, seg3)
88      variable no_dp : integer := 0;
89  begin
90      no_dp := no_dp + 1;
91
92      if (no_dp = 1) then
93          dp <= "1110";
94      elsif (no_dp = 2) then
95          dp <= "1101";
96      elsif (no_dp = 3) then
97          dp <= "1011";
98      elsif (no_dp = 4) then
99          dp <= "0111";
100      else
101          dp <= "1111";
102          no_dp := 0;
103      end if;
104  end process dp_proc;

```

Fig. 4.4 Simulation Result and Test Bench

5. FOUR-BIT RIPPLE-CARRY ADDER

OVERVIEW

A ripple carry adder is a logic circuit in which the carry-out of each full adder is the carry in of the succeeding next most significant full adder. Full adder is a logic circuit that adds two input operand bits plus a Carry in bit and outputs a Carry out bit and a sum bit.

VHDL CODE

```
1  -- full_adder define
2  library IEEE;
3  use IEEE.std_logic_1164.ALL;
4
5  entity full_adder is
6      port (
7          a, b, cin : in std_logic;
8          sum, cout: out std_logic
9      );
10 end full_adder;
11
12 architecture behavior of full_adder is
13 begin
14     sum <= (a XOR b) XOR cin;
15     cout <= (a AND b) or (a AND cin) or (b AND cin);
16 end behavior;
```

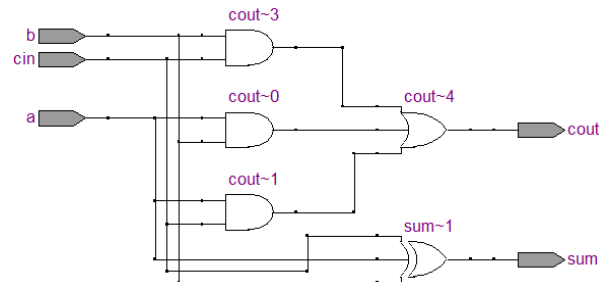


Fig. 5.1 Full Adder block and Code

```
22 entity nbit_adder is
23     generic ( N : natural := 4); -- initialize 4-bit adder
24     port(
25         A, B : in std_logic_vector(N-1 downto 0);
26         Cin : in std_logic;
27         Sum : out std_logic_vector(N-1 downto 0);
28         Cout : out std_logic
29     );
30 end nbit_adder;
31
32 architecture behavior of nbit_adder is
33     component full_adder
34         port(
35             a, b, cin : in std_logic;
36             sum, cout: out std_logic
37         );
38     end component;
39     signal co : std_logic_vector(N downto 0);
40 begin
41     co(0) <= Cin;
42     Cout <= co(N-1);
43
44     GEN: for i in 0 to N-1 generate
45         nb_adder: full_adder port map (A(i), B(i), co(i),
46                                         Sum(i), co(i+1) );
47     end generate GEN;
48
49 end behavior;
```


 


Fig. 5.2 Four-Bit Full Adder Block and Code

SIMULATION

 

```

51  -- Stimulus process
52  stim_proc: process
53  begin
54      wait for 50 ns;
55      A <= A+1;
56      B <= B+3;
57      Cin <= not Cin;
58  end process;

```

Fig. 5.3 Simulation result and test bench


6. FOUR-BIT RIPPLE-CARRY ADDER/SUBTRACTOR

OVERVIEW


An adder-subtractor is a circuit that is capable of adding or subtracting numbers. A 4-bit ripple-carry adder-subtractor based on a 4-bit adder that performs two's complement on **A** when **MOD = 1** to yield **Sum = B - A**.

VHDL CODE

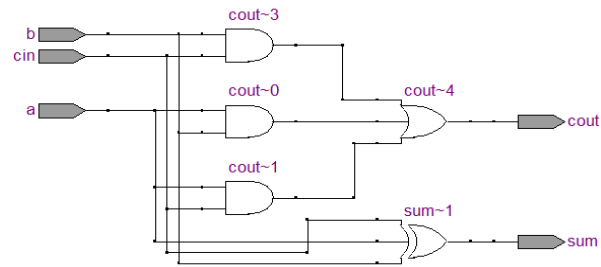
```
1  -- full_adder define
2  library IEEE;
3  use ieee.std_logic_1164.ALL;
4
5  entity full_adder is
6      port (
7          a, b, cin : in std_logic;
8          sum, cout: out std_logic
9      );
10 end full_adder;
11
12 architecture behavior of full_adder is
13 begin
14     sum <= (a XOR b) XOR cin;
15     cout <= (a AND b) or (a AND cin) or (b AND cin);
16 end behavior;
```



```
22 entity add_sub is
23     generic ( N : natural := 4); -- initialize 4-bit adder/subtractor
24     port(
25         A, B : in std_logic_vector(N-1 downto 0);
26         Mode : in std_logic;
27         Sum : out std_logic_vector(N-1 downto 0);
28         Cout : out std_logic
29     );
30 end add_sub;
31
32 architecture fbas_arc of add_sub is
33     component fulladder
34         port(
35             a, b, cin : in std_logic;
36             sum, cout: out std_logic
37         );
38     end component;
39     signal co : std_logic_vector(N downto 0);
40     signal xorB : std_logic_vector(N-1 downto 0);
41 begin
42     co(0) <= Mode;
43     Cout <= co(N-1);
44
45     SUB: for i in 0 to N-1 generate
46         mod_b: xorB(i) <= B(i) XOR Mode;
47     end generate SUB;
48
49     GEN: for i in 0 to N-1 generate
50         nb_adder: fulladder port map(A(i), xorB(i), co(i),
51                                     Sum(i), co(i+1) );
52     end generate GEN;
53 end fbas_arc;
```

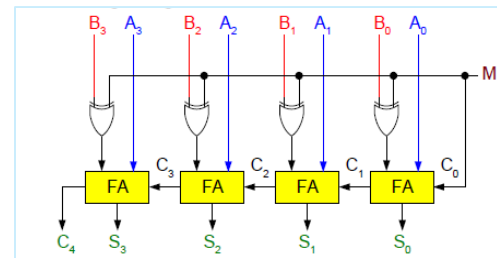

SIMULATION

 

```

50  -- Stimulus process
51  ab_proc: process
52  begin
53      wait for 100 ns;
54      A <= A+2;
55      B <= B+3;
56  end process;
57
58  mode_proc: process
59  begin
60      wait for 50 ns;
61      Mode <= not Mode;
62  end process;

```

Fig. 6.1 Simulation result and test bench

CONCLUSION

In this coursework, I have designed, implemented a **32 bit ALU**, a **Mux16to4**, a **BCDto7Segment Display**, a **Four-digit 7-Segment Display Decoder**, a **4-Bit Ripple-Carry Adder**, and **4-bit Ripple-Carry Adder/Subtractor**.

All the above design are then verified to see whether they match theoretically or not. All above given simulation waveforms show that they match completely thereby verifying our desired results.

Through this coursework, I have mastered the basic VHDL programming skills and simulation test bench method.

REFERENCES

- [1]. <https://www.youtube.com/watch?v=r8xVQ3ThQK8>
- [2]. Geetanjali, Nishant Tripathi, VHDL Implementation of 32-Bit Arithmetic Logic Unit (Alu)
- [3]. <http://vhdlguru.blogspot.no/2011/06/vhdl-code-for-simple-alu.html>
- [4]. https://en.wikipedia.org/wiki/Arithmetic_logic_unit
- [5]. <https://en.wikipedia.org/wiki/Adder%E2%80%99subtractor>
- [6]. [https://en.wikipedia.org/wiki/Adder_\(electronics\)](https://en.wikipedia.org/wiki/Adder_(electronics))
- [7]. <http://ece320web.groups.et.byu.net/labs/Lab3-SevenSegmentDisplay/SevenSegmentDecoder.html>
- [8]. Spartan-3 Starter Kit Board User Guide
<http://ece320web.groups.et.byu.net/resources/S3BOARD-rm.pdf>
- [9]. Nexys3 Reference Manual Revision: April 10, 2013
- [10]. http://www.electronics-tutorials.ws/combinational/comb_6.html
- [11]. <https://en.wikipedia.org/wiki/Multiplexer>
- [12]. <http://www.circuitstoday.com/ripple-carry-adder>
- [13]. <http://1.bp.blogspot.com/-Jq5PICZle18/TsLQcUfUe4I/AAAAAAAAANK/71sLNGItC3s/s1600/Capture6.PNG>

APPENDICES



- [1]. VHDL Source Code : VHDL_ASG.rar